



RISC-V Processor

Carlos Ornelas

CECS 440 - Computer Architecture

Supervisor/Professor: Dr. Seyyedhosseini

California State University Long Beach College of Engineering



Table of Contents

Overview	1
Development	2
Processor Design	3
Schematic	3
Detailed Description	3
I/O Signal Chart	4
Controller Design	5
Schematic	5
Detailed Description	5
I/O Signal Chart	6
ALU Controller Design	7
Schematic	7
Detailed Description	7
I/O Signal Chart	7
Datapath Design	8
Schematic	8
Detailed Description	9
I/O Signal Chart	9
Flip Flop	10
Schematic	10
Detailed Description	10
I/O Signal Chart	10
Instruction Memory	11
Schematic	11
Detailed Description	11
I/O Signal Chart	11
32 x 32 Register File	12
Schematic	12
Detailed Description	12
I/O Signal Chart	13
Immediate Value Generator	14
Schematic	14
Detailed Description	14
I/O Signal Chart	14

ALU (Arithmetic Logic Unit)	15
Schematic	15
Detailed Description	15
I/O Signal Chart / ALU Operation Codes	16
Data Memory	18
Schematic	18
Detailed Description	18
I/O Signal Chart	18
Simulation/Verification	19
Verilog	21
References	22


1. Overview

This report provides a technical description and guide in creating a Single Cycle 32-Bit RISC-V processor using Verilog in the Vivado Suite. The processor is made up of three modules: the datapath, the ALU controller, and the controller. The datapath is the main brain of the system and contains important building blocks like the 32 x 32 Register and the ALU. Next, is the controller which basically determines the source operand, as well as determining if data will be read/written to the memory and registers. Lastly, The ALU controller selects what operation will be performed by the ALU in the datapath.

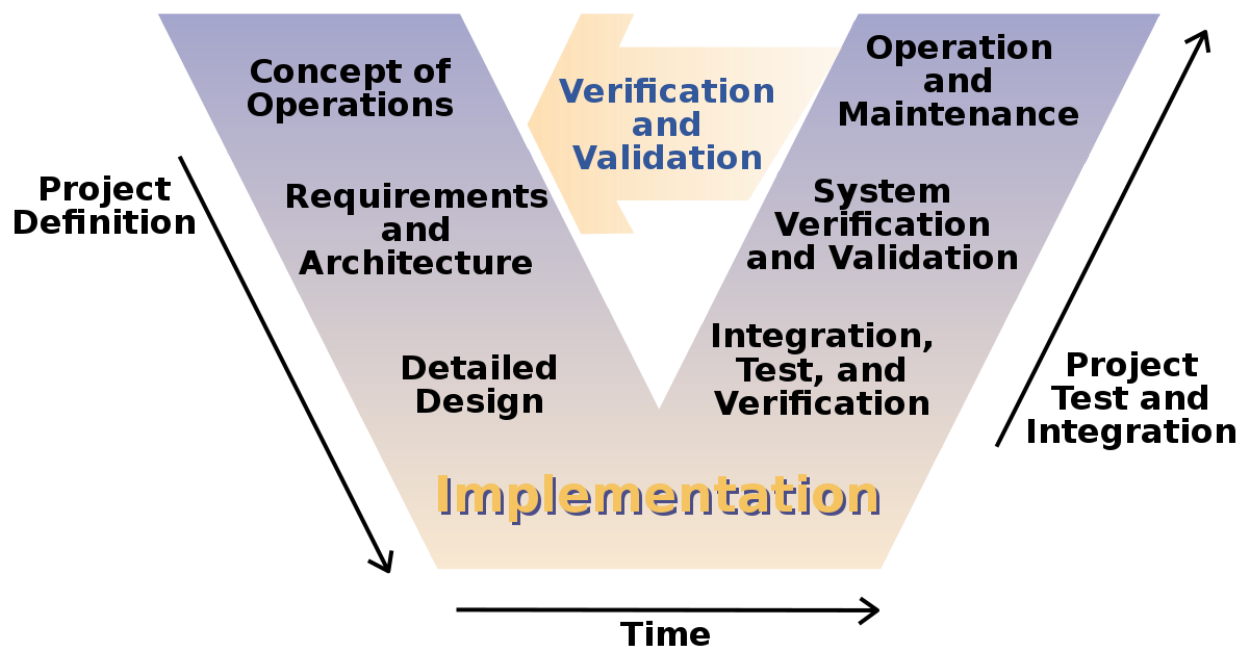2. Development


For this project I used Xilinx's Vivado suite. The Vivado suite is the successor to the Xilinx ISE design suite. This was developed alongside the class using lecture notes and some guidance from professor Dr. Seyyedhosseini. Adding onto the project I will be creating a separate github folder that will contain the function of the processor, but tested on a Nexys 4 FPGA.

The Development process loosely followed the guidelines of the commonly known V diagram. The project definition portion of the project was given to us by Dr. Seyyedhosseini, while the build and test portions of the V diagram was done independently. The V-model project flow is below.



3. Processor Design

3.1. Schematic

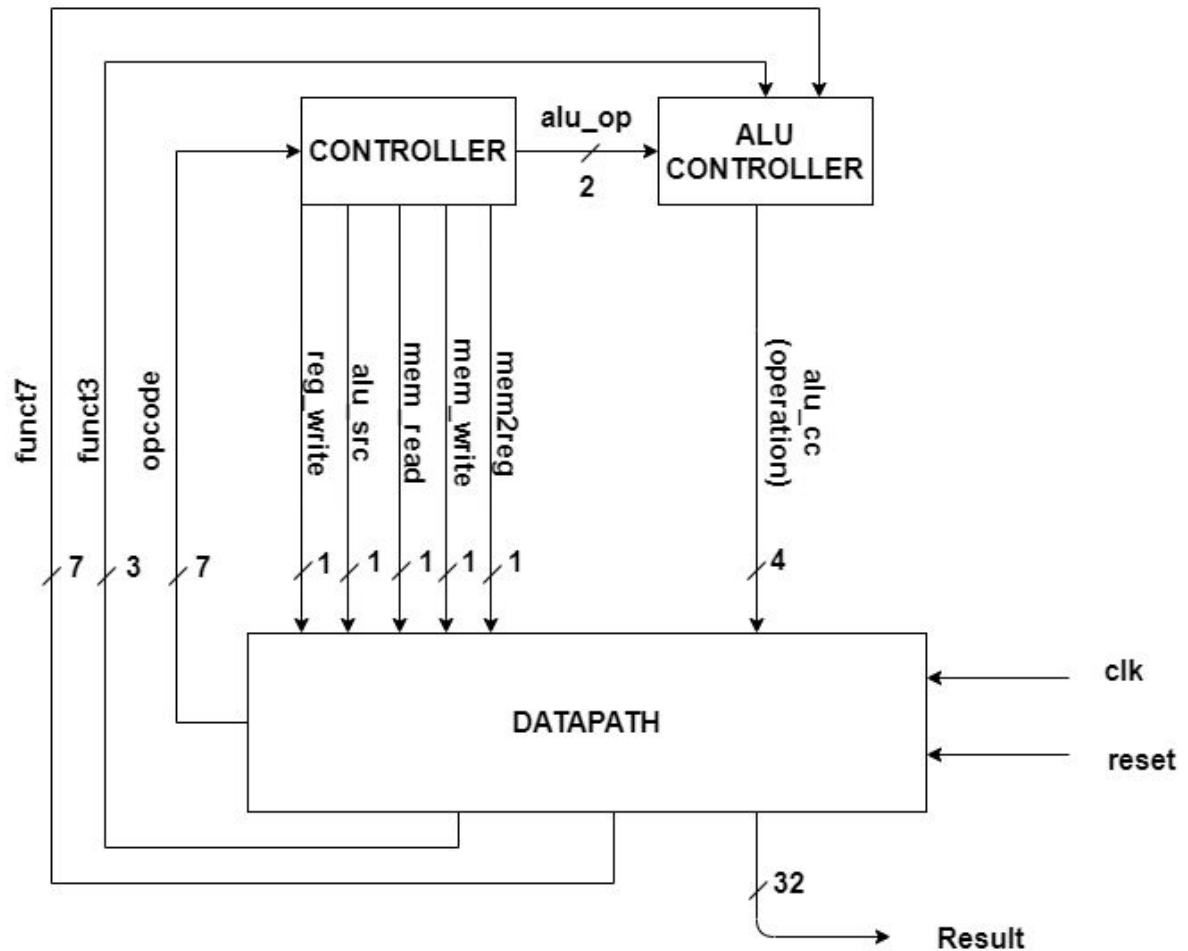

3.2. Detailed Description


Top module for the design. The processor holds the three main modules and connects them to each other. The modules are the following: ALUController, Controller, and Datapath. As mentioned previously, this processor is based around the RISC-V architecture and is a single cycle design.

3.3. I/O Signal Chart

Signal	I/O	Size	Description
clk	Input	1	System wide clock. Synchronous.
reset	Input	1	System wide reset. Sets registers and other blocks back to “default” state.
Result	Output	32	Final result of the processor. Usually a result from the ALU, but could also be values from registers and memory.

4. Controller Design

4.1. Schematic

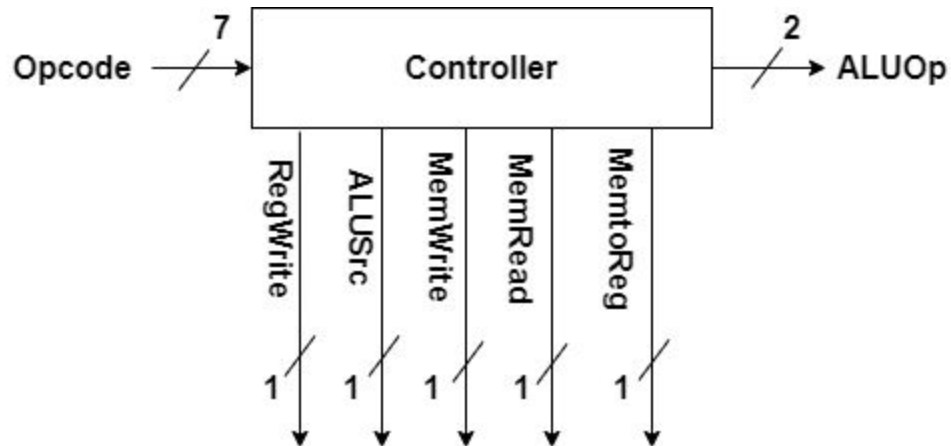

4.2. Detailed Description

The control unit is responsible for determining what operation that the ALU controller will further specify. Furthermore, it tells the datapath whether it will be performing a simple arithmetic operation, storing/loading data, or writing/reading data. The way the Controller determines this is by taking the opcode from the datapath and decoding it based around the truth table below. The truth table was provided by the professor and was created in conjunction with the RISC-V datasheet.

Table 1 : Control Signals.


		Opcode			
		0110011	0010011	0000011	0100011
		AND, OR, ADD, SUB, SLT, NOR	ANDI, ORI, ADDI, SLTI, NORI	LW	SW
Control Signals	MemtoReg	0	0	1	0
	MemWrite	0	0	0	1
	MemRead	0	0	1	0
	ALUSrc	0	1	1	1
	Regwrite	1	1	1	0
	ALUOp	10	00	01	01

4.3. I/O Signal Chart

Signal	I/O	Size	Description
Opcode	Input	7	The opcode is the first 7 bits (LSB) of the 32 bit instruction taken from the instruction memory within datapath. The opcode location is determined by the RISC-V processor manual.
RegWrite	Output	1	This signal determines whether the register file in the datapath gets written to or not.
ALUSrc	Output	1	This signal determines whether one of the ALU's operands comes from the 32 x 32 register file or the immediate generator. Generated by decoding the opcode.
MemWrite	Output	1	Write enable signal for writing to memory in the datapath.
MemRead	Output	1	Read-enable signal for reading from memory in the datapath.
MemtoReg	Output	1	Signal that goes to a multiplexor which determines whether the result of the ALU or the output from memory goes to the register.
ALUOp	Output	2	Gets sent to the ALU and determines what operation the ALU will perform.

5. ALU Controller Design

5.1. Schematic

 

5.2. Detailed Description


The ALU Controller is a second controller used to access more specific ALU operations if needed. Along with the ALUOp input, the Funct7 and Funct3 inputs can access different operations along the tree of the general ALUOp given. These specified operations are defined in the RISC-V datasheet.

5.3. I/O Signal Chart

Signal	I/O	Size	Description
ALUOp	Input	2	The Alu Operation to be performed. Received from the Controller.
Funct7	Input	7	Helps define the function further if needed. Relegated to R-type instructions.
Funct3	Input	3	3 bit function selector. Helps define the operation further.
Operation	Output	4	The fully defined operation to be performed

6. Datapath Design

6.1. Schematic

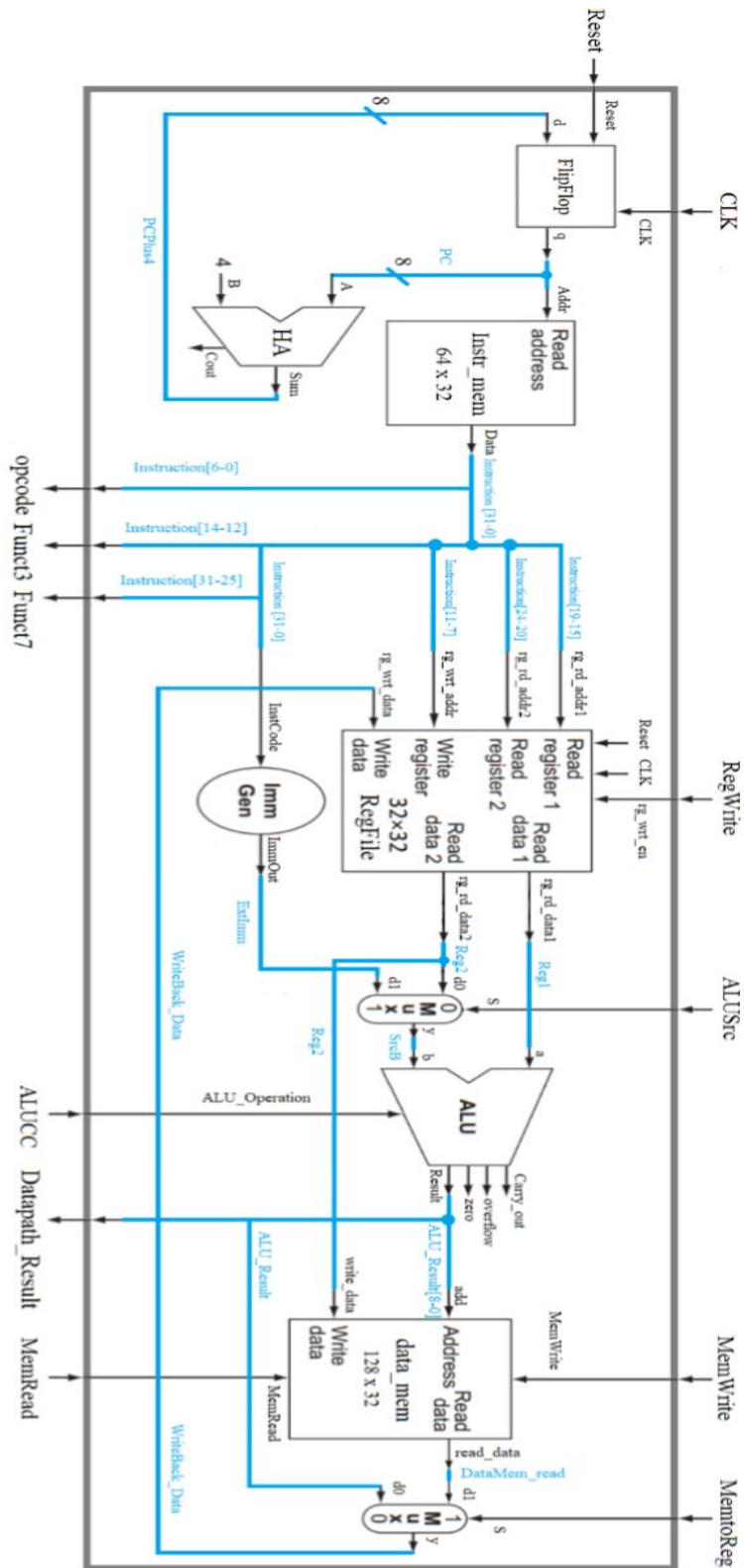

6.2. Detailed Description


As the name suggests, the datapath is where operations are fetched and executed. The main brain of the processor, where the ALU, register file, instruction memory, and data memory lives.

6.3. I/O Signal Chart

Signal	I/O	Size	Description
clk	Input	1	System wide clock
reset	Input	1	System wide reset sets all inputs to default state
reg_write	Input	1	Input to enable the write-to-register signal in the Register file.
mem2reg	Input	1	Mux Selector for the second multiplexor
alu_src	Input	1	Mux selector for the first multiplexor
mem_write	Input	1	Enables the write to memory signal for the data memory module
mem_read	Input	1	Enables the read from memory signal for the data memory module
alu_cc	Input	4	Alu Operation selection for the ALU module
opcode	Output	7	Operation code. Is sent to the controller to be decoded and then sent to the ALU controller.
funct7	Output	7	Is sent to the ALU controller to be decoded. Specifies the ALU operation to be performed.
funct3	Output	3	Is sent to the ALU controller to be decoded. Specifies the operation further.
alu_result	Output	32	Result from the ALU.

6.3.1. Flip Flop

6.3.1.1. Schematic

 

6.3.1.2. Detailed Description


This is a Synchronous D Flip Flop. Reset will only reset values to zero upon at every positive edge clock signal. If reset is inactive, then at every positive edge of the clock q gets all 8 bits of d. The flip flop is used to hold each new memory address at each positive edge of the clock. To move to a new memory location the current memory location must be added by 4, as each memory location is 4 bytes wide.

6.3.1.3. I/O Signal Chart

Signal	I/O	Size	Description
clk	Input	1	Positive Edge Clock
reset	Input	1	Synchronous Reset
d	Input	8	Holds the new memory address from the half adder.
q	Output	8	Receives the input if reset is inactive and sends to the half adder to go to the next memory location

6.3.2. Instruction Memory

6.3.2.1. Schematic

 

6.3.2.2. Detailed Description


Instruction Memory works like a pointer, as the purpose for the module is to hold all the necessary instructions in memory. Within the instruction memory module, we have simulated a two-dimensional 32 x 64 memory module.

6.3.2.3. I/O Signal Chart

Signal	I/O	Size	Description
Address	Input	8	The location of the instruction in memory. We get the address from the flip flop.
Instruction	Output	32	The 32 bit instruction being pointed at.

6.3.3. 32 x 32 Register File

6.3.3.1. Schematic

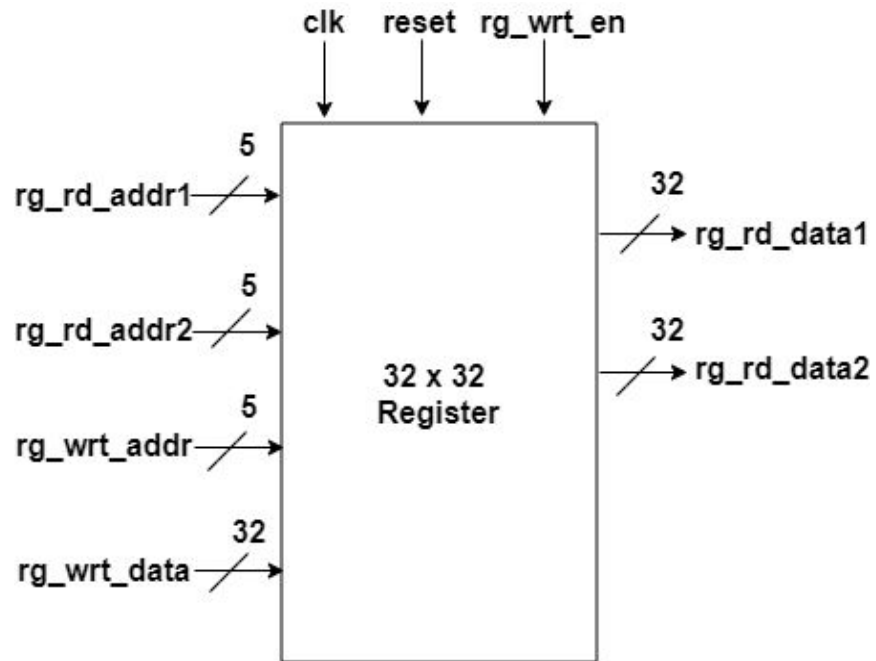

6.3.3.2. Detailed Description


An asynchronous 32x32 register module. This register block can be written and read from. When write enable is low then the register block cannot be written to, however when enabled then the data from rg_wrt_data will be written to the location defined in rg_wrt_addr. The two read address inputs each correspond to the rg_rd_data outputs after data had been read from the address.

6.3.3.3. I/O Signal Chart

Signal	I/O	Size	Description
clk	Input	1	Clock signal
reset	Input	1	Asynchronous reset
rg_wrt_en	Input	1	Active high enable
rg_rd_addr1	Input	5	Address to read data from to be sent to rg_rd_data1
rg_rd_addr2	Input	5	Address to read data from to be sent to rg_rd_data2
rg_wrt_addr	Input	5	Address to be written to.
rg_wrt_data	Input	32	Data to be written to specified address
rg_rd_data1	Output	32	Data read from the register. Will be sent to the “A” operand for the ALU
rg_rd_data2	Output	32	Data read from the register. Will be sent to the “B” operand for the ALU.

6.3.4. Immediate Value Generator

6.3.4.1. Schematic

 

6.3.4.2. Detailed Description


Decodes the instruction code and determines if the immediate value needs to be sign-extended to 32 bits in order to properly perform the operation without error.

6.3.4.3. I/O Signal Chart

Signal	I/O	Size	Description
Instruction Code	Input	32	The full 32-bit instruction code from instruction memory
Immediate Out	Output	32	The sign-extended value

6.3.5. ALU (Arithmetic Logic Unit)

6.3.5.1. Schematic

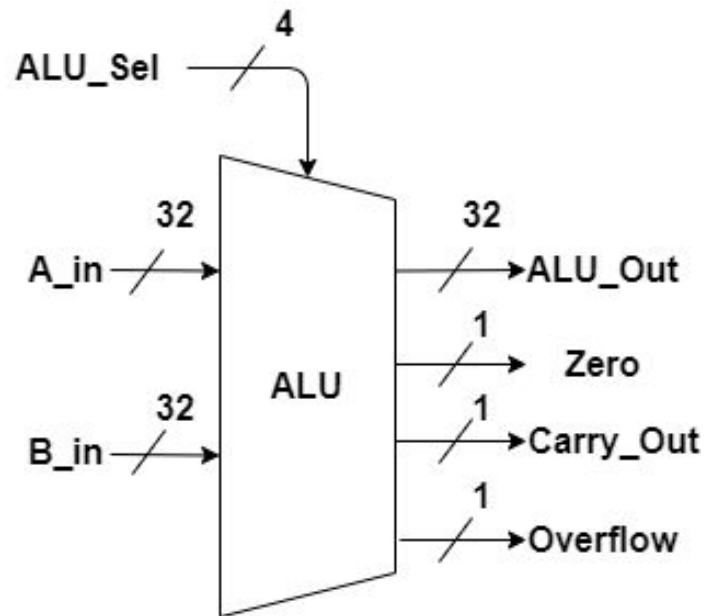

6.3.5.2. Detailed Description

This is a 32-Bit ALU module abstraction, not built for any particular FPGA. An ALU is an arithmetic logic unit and is often called the “brain” of the computer. An ALU performs logical and arithmetic operations depending on what the designer included, as well as what operation is being selected.

This ALU has two 32-bit inputs and a total of 7 operations **(detailed below)** using a 4-bit opcode selection. Furthermore, This ALU also includes 3 forms Status checks: Zero, Carry-Out, and Overflow. The first operand's data, A_in, comes from the rg_rd_addr1 signal. On the other hand, the second operand, B_in, gets its data from either the rg_rd_addr2 signal or the Immediate Out signal. This is selected using a 2 to 1 Mux **(Shown below)** where the ALU_Src (select signal) comes from the Controller. Active high “1” to select the Immediate Out signal and vice versa for the rg_rd_addr2 signal.

6.3.5.3. I/O Signal Chart / ALU Operation Codes


Signal	I/O	Size	Description
A_in	Input	32	1st operand. Comes from rg_rd_addr1.
B_in	Input	32	2nd operand. Comes from either rg_rd_addr2 or the Immediate generator.
ALU_Sel	Input	4	Operation Selection. 7 operations total. 4-bit length size.
ALU_Out	Output	32	32-bit result of the operation on the two operands
Carry_Out	Output	1	1-bit status flag. If Carry_Out is a 1 it means that the result had a carry out on the MSB
Overflow	Output	1	1-bit status flag. If Overflow is a 1 it means that the result of the operation could not fit in the 32-bit register
Zero	Output	1	1-bit status flag. If Zero is “on” then all 32- bits of ALU_Out are zero.

ALU OPERATION CODES

ALU Control Line	Function	Description
0000	AND	Boolean And operation
0001	OR	Boolean or operation
0010	ADD	Adds both operands
0110	SUBTRACT	Subtract both operands
0111	SET LESS THAN	If A_in is less than B_in then ALU_Out is a 1, else 0
1100	NOR	Boolean NOR operation
1111	EQUAL COMPARE	If A_in and B_in are equal, then ALU_Out is a 1, else 0

6.3.6. Data Memory

6.3.6.1. Schematic

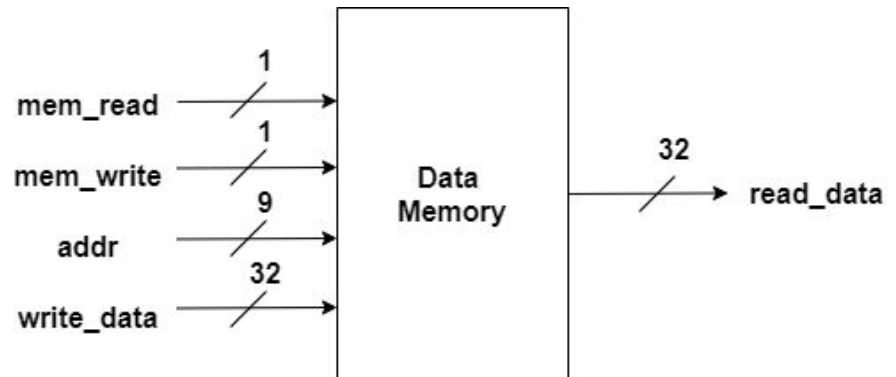

6.3.6.2. Detailed Description


Holds the result from the ALU. The memory size is 128x32 and is byte accessible.



6.3.6.3. I/O Signal Chart

Signal	I/O	Size	Description
mem_read	Input	1	Active high signal to initiate the read process.
mem_write	Input	1	Active high signal to initiate the write process
addr	Input	9	Memory address to read or write from
write_data	Input	32	Data to be written to memory
read_data	Output	32	Data read from memory

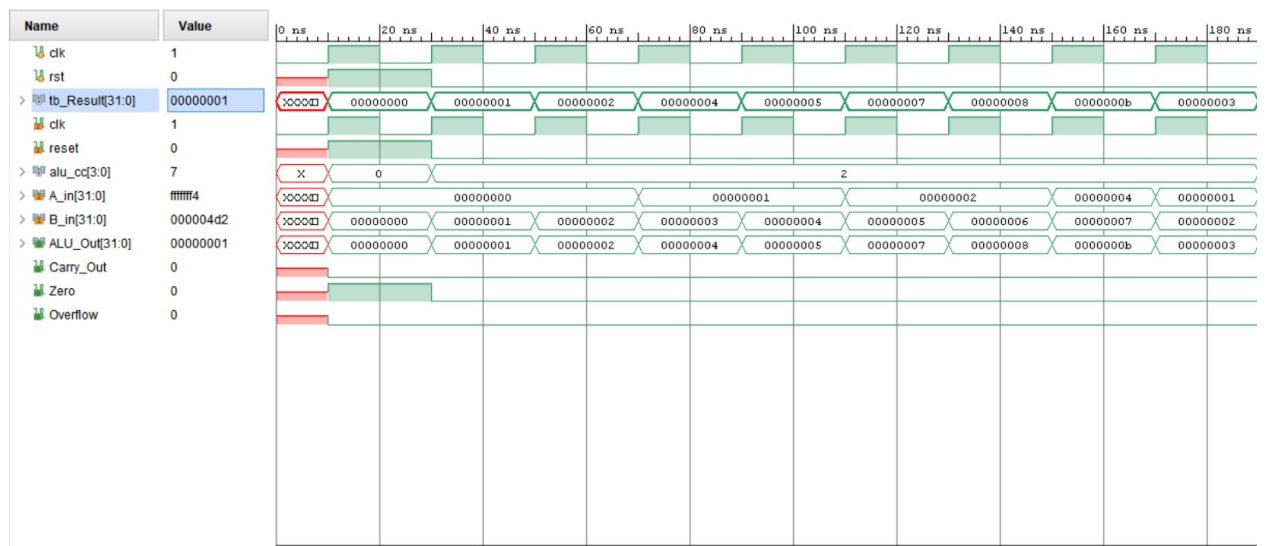7. Simulation/Verification

The waveforms test each instruction of the processor at each clock cycle and show the status flags working dependent on what the output is.



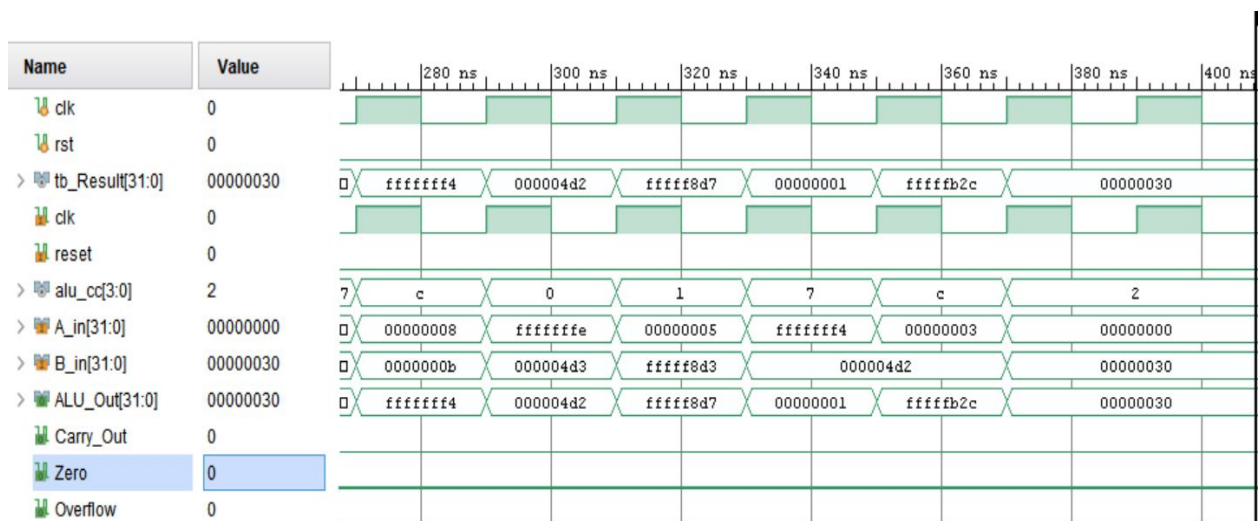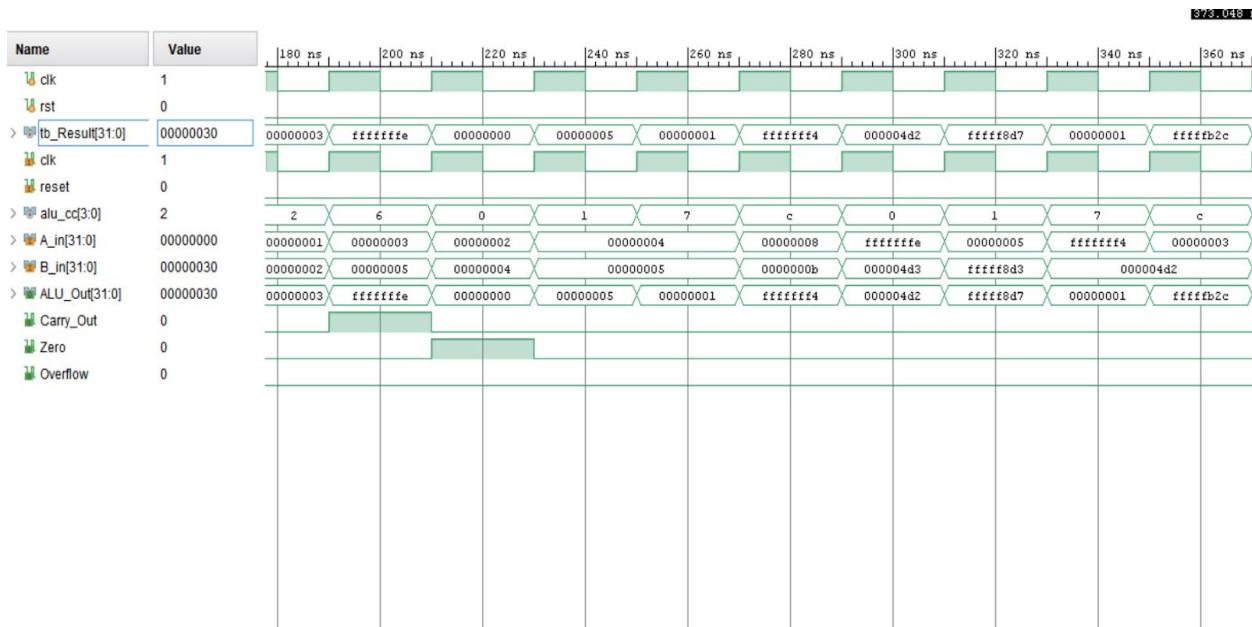

8. Verilog

Please refer to the following Git repository for the Verilog.

Please refer to the README in the repository.

https://github.com/skecherboy/RISC-V_Processor_32Bits

9. References

<https://riscv.org/technical/specifications/>

Dr. Seyyedhosseini's lectures and code examples.